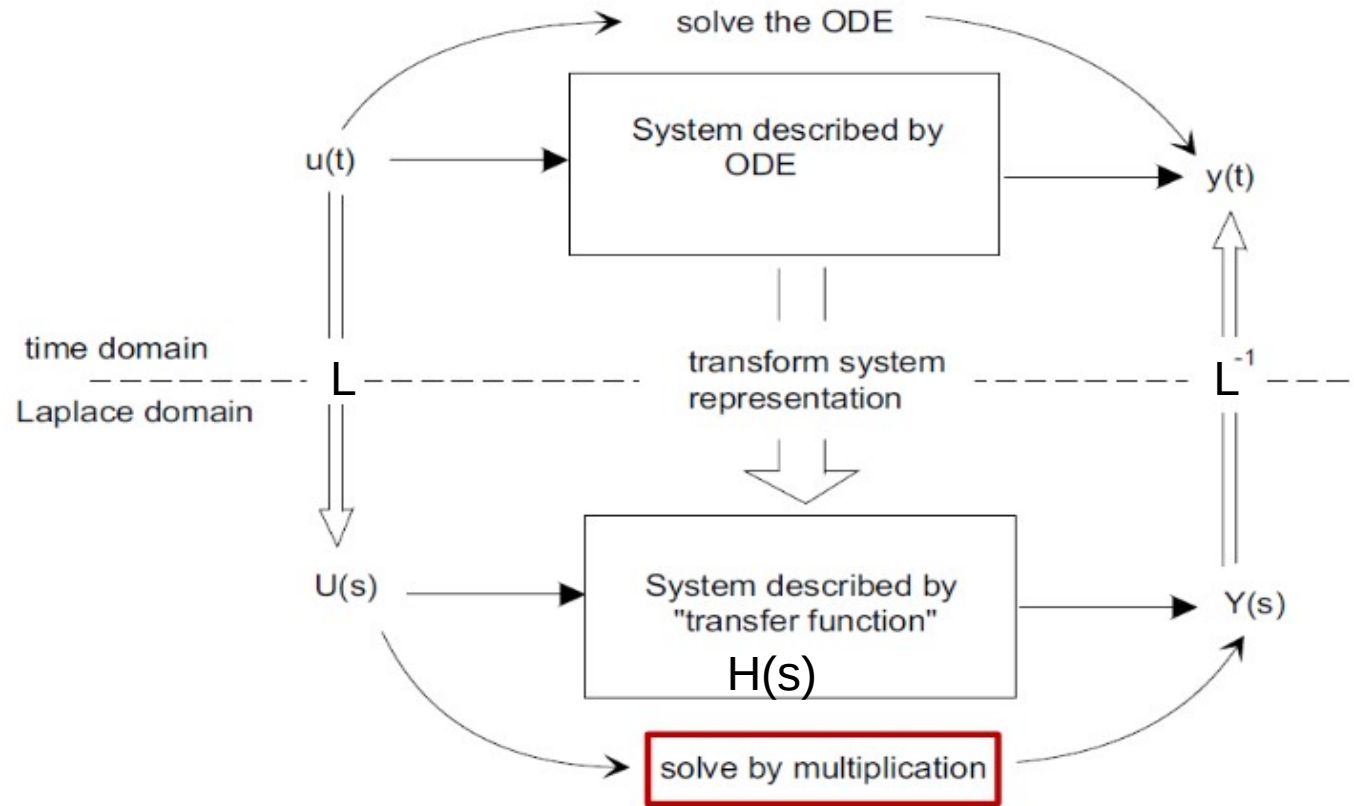


Analog IC Design


Lecture 2 circuits and systems review

Laplace Transform (LT)



Laplace Transform (LT)

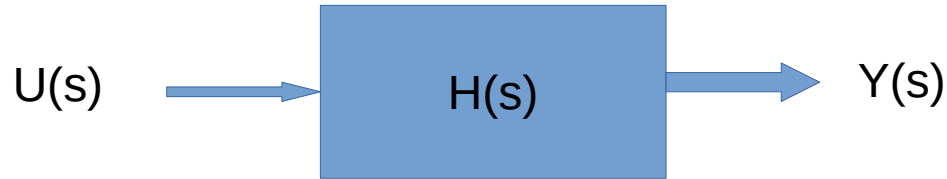- Laplace transform helps you to solve differential equations by multiplication and division



$$Y(s) = H(s)U(s)$$

$$H(s) = \frac{Y(s)}{U(s)}$$

Laplace Transform (LT)

Time domain	Laplace domain
e^{at}	$\frac{1}{s-a}$
$\int_0^t f(t)dt$	$\frac{1}{s}F(s)$
$\frac{df(t)}{dt}$	$sF(s)$
$\delta(t)$	1
$u(t)$	$\frac{1}{s}$

System input	System response (output) in Laplace domain
Unit impulse: $\delta(t)$	$H(s)$
Unit step: $u(t)$	$\frac{1}{s}H(s)$

Poles and Zeros



- Transfer function
- Zeros: roots of the numerator $N(s) = 0$
- Poles: roots of the denominator (characteristic eq.) $D(s) = 0$
- For physical systems, poles & zeros are real or complex conjugate

$$H(s) = \frac{N(s)}{D(s)}$$

Notes:


- If the system input is impulse in the time domain then the output is the transfer function in laplace domain

Real and Complex Poles

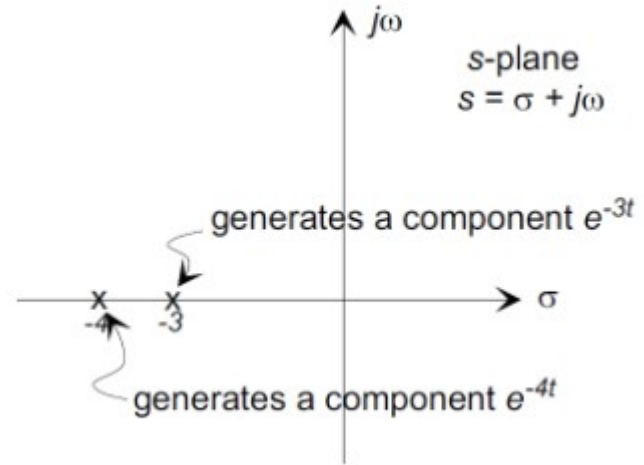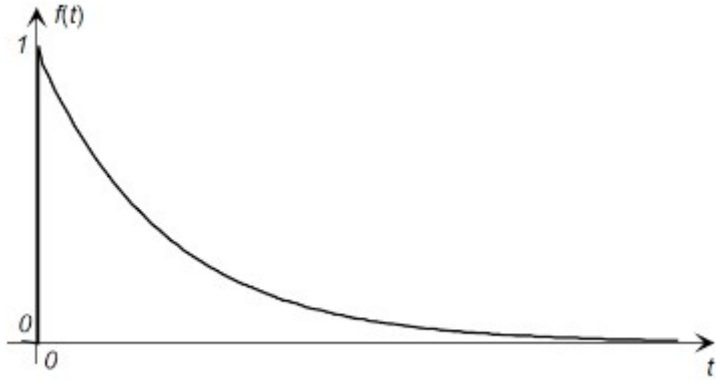

LHP and RHP Poles

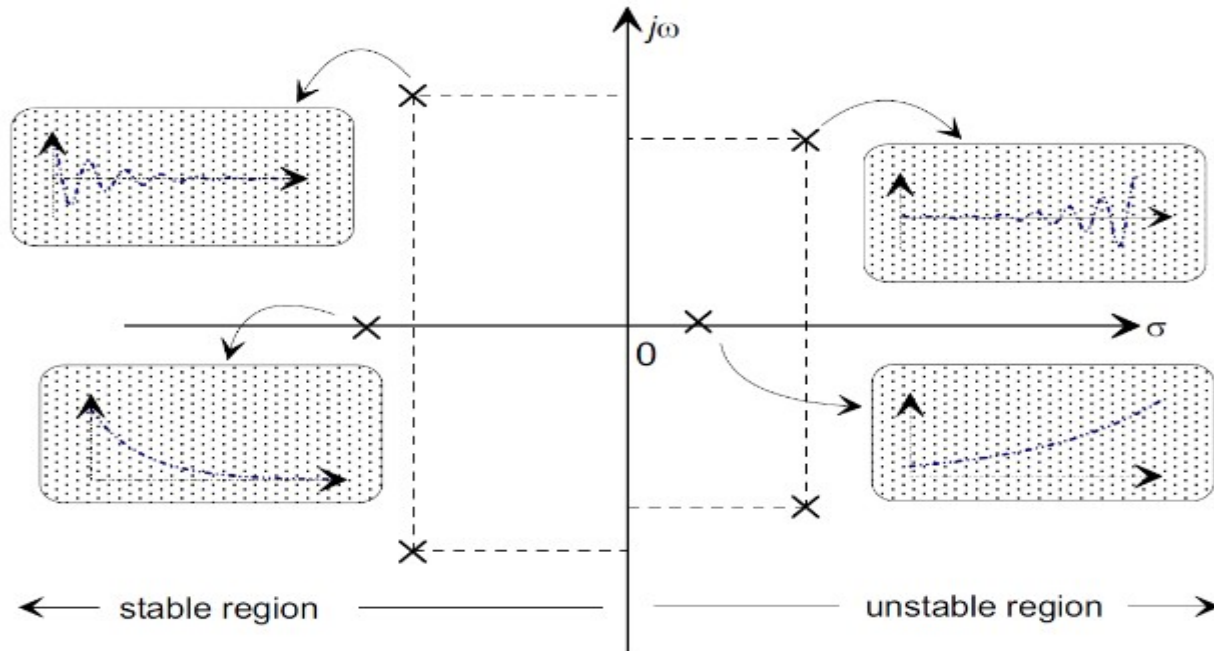- Poles in LHP: Decaying exponential (stable system)
- Poles in RHP: Growing exponential (unstable system)



First-Order LPF

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{1/sC}{R + 1/sC} = \frac{1}{1 + sRC} = \frac{1}{1 + s\tau}$$
$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{1/j\omega C}{R + 1/j\omega C} = \frac{1}{1 + j\omega RC} = \frac{1}{1 + \frac{j\omega}{\omega_c}}$$


- $\tau = RC$: time constant
- $\omega_c = \frac{1}{\tau} = \frac{1}{RC}$: cutoff/corner frequency

Poles: $s_p = -\frac{1}{\tau} = -\omega_c$



Zeros: ? @ $\omega = \infty$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$
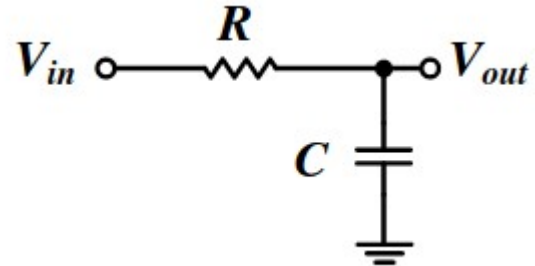
$$P(H(j\omega)) = -\tan^{-1} \frac{\omega}{\omega_c}$$



First-Order LPF Bode Plot

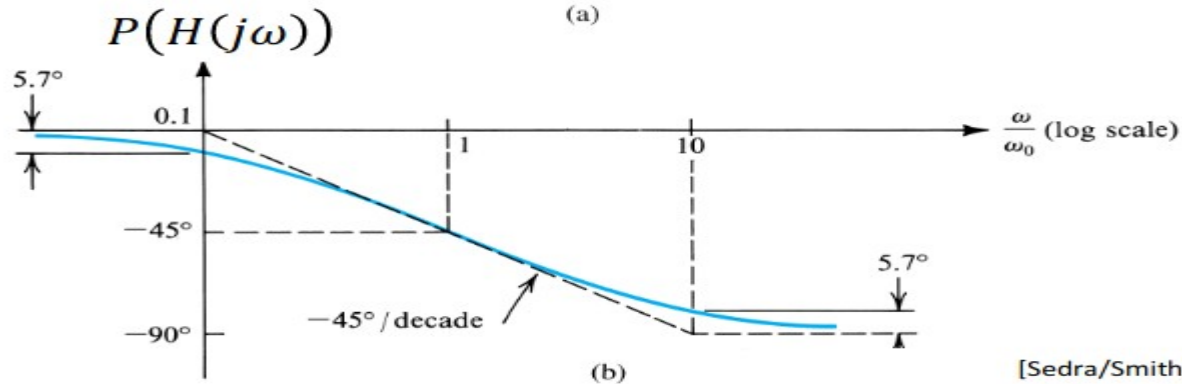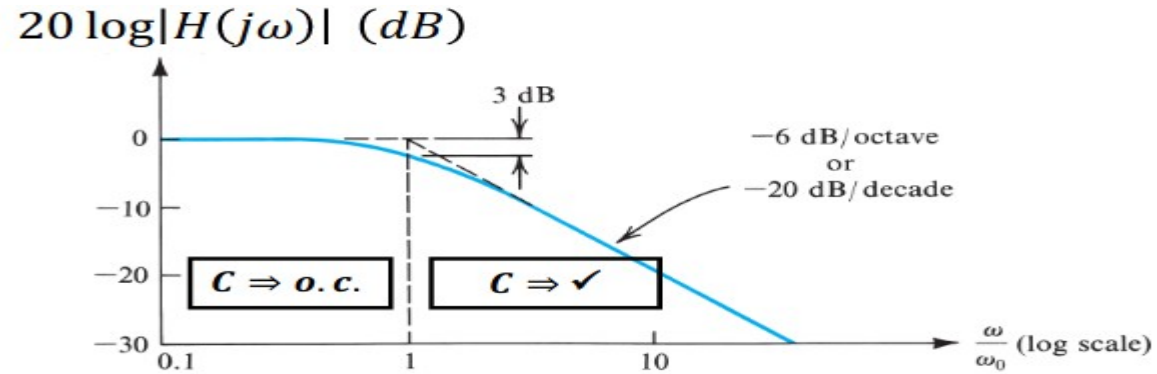

[Sedra/Smith, 2015]

First-Order HPF

$$H(s) = \frac{v_{out}(s)}{v_{in}(s)} = \frac{R}{R + 1/sC} = \frac{sRC}{1 + sRC} = \frac{s\tau}{1 + s\tau}$$


$$H(j\omega) = \frac{v_{out}(j\omega)}{v_{in}(j\omega)} = \frac{R}{R + 1/j\omega C} = \frac{j\omega RC}{1 + j\omega RC} = \frac{\frac{j\omega}{\omega_c}}{1 + \frac{j\omega}{\omega_c}}$$

❑ Poles: $s_p = -\frac{1}{\tau} = -\omega_c$


❑ Zeros: $s_z = 0$

❑ $|H(j\omega)| = \frac{\frac{\omega}{\omega_c}}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$

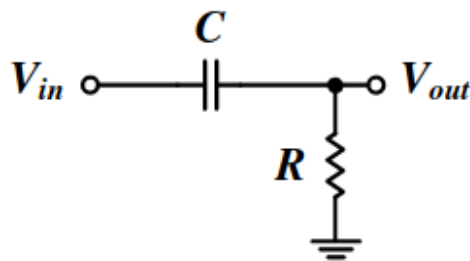
❑ $P(H(j\omega)) = 90^\circ - \tan^{-1} \frac{\omega}{\omega_c}$



First-Order HPF Bode Plot

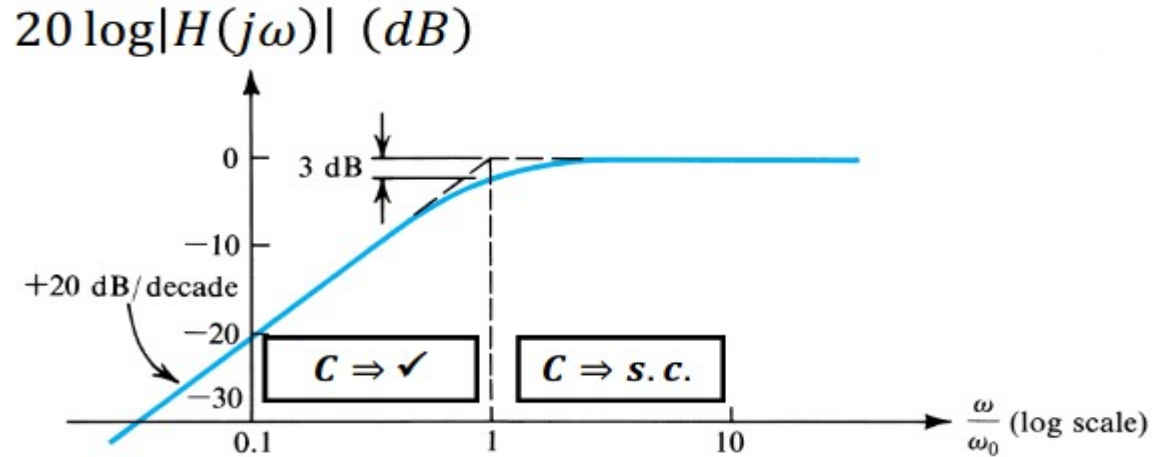

(a)

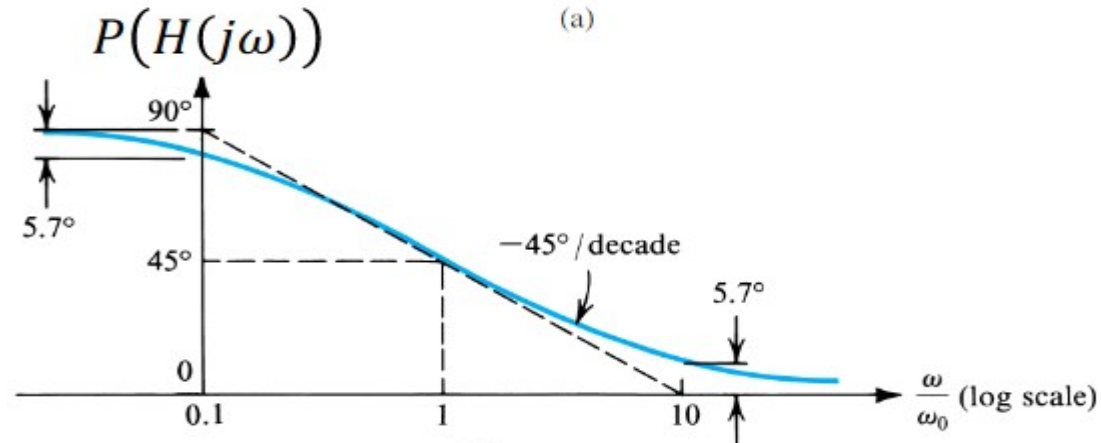

(b)


Second-Order System: LC LPF

$$H(s) = \frac{Z_C}{R + Z_L + Z_C} = \frac{1}{LCs^2 + RCs + 1}$$

$$\omega_o^2 = \frac{1}{LC} \quad \text{and} \quad Q = \frac{\omega_o L}{R} = \frac{1}{\omega_o RC} = \frac{1}{2\zeta}$$

□ Higher R means higher damping (ζ) and lower quality factor (Q)
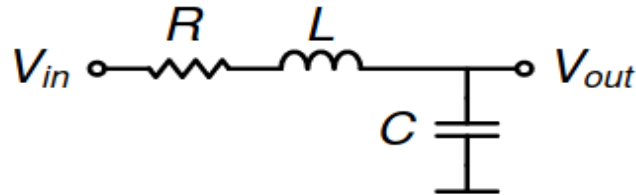
$$H(s) = \frac{1}{\left(\frac{s}{\omega_o}\right)^2 + \frac{s}{\omega_o Q} + 1} = \frac{\omega_o^2}{s^2 + \left(\frac{\omega_o}{Q}\right)s + \omega_o^2} = \frac{\omega_o^2}{s^2 + (2\zeta\omega_o)s + \omega_o^2}$$




Second-Order Passive LC LPF

$$H(s) = \frac{1}{\left(\frac{s}{\omega_o}\right)^2 + \frac{s}{\omega_o Q} + 1} = \frac{\omega_o^2}{s^2 + \left(\frac{\omega_o}{Q}\right)s + \omega_o^2}$$

□ The poles occur at $s^2 + \left(\frac{\omega_o}{Q}\right)s + \omega_o^2 = 0$
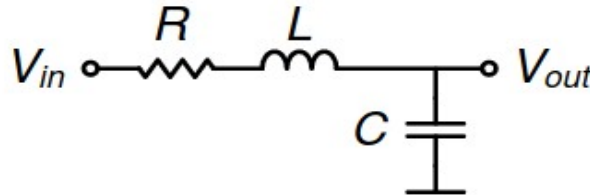
$$s_{p1,2} = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a} = -\frac{\omega_o}{2Q} \pm \frac{\omega_o}{2} \sqrt{\frac{1}{Q^2} - 4}$$




Second-Order System Poles

$$H(s) = \frac{1}{\left(\frac{s}{\omega_o}\right)^2 + \frac{s}{\omega_o Q} + 1} = \frac{1}{\left(\frac{s}{\omega_o}\right)^2 + \frac{s}{\omega_o/2\zeta} + 1}$$

$$s_{p1,2} = -\frac{\omega_o}{2Q} \pm \frac{\omega_o}{2} \sqrt{\frac{1}{Q^2} - 4}$$

$= \frac{1}{2}$

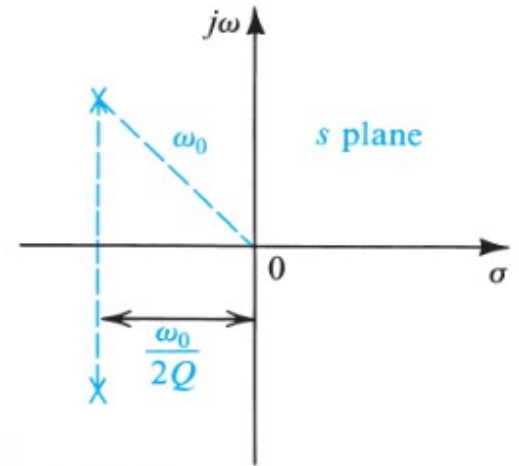


❑ If $Q < 0.5$ ($\zeta > 1$): overdamped system, roots are real, negative, and distinct, like two first-order RC filters in cascade



❑ If $Q = 0.5$ ($\zeta = 1$): critical damped system, roots are real, negative, and equal



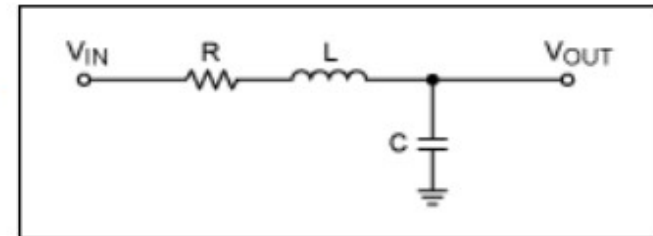❑ If $Q > 0.5$ ($\zeta < 1$): underdamped system, roots are complex conjugate




Ring and Peaking

- 1) $Q < 0.5$ ($\zeta > 1$): over damped system roots are real, negative, and distinct
- 2) $Q = 0.5$ ($\zeta = 1$): critical damped system, roots are real, negative, and equal
- 3) $Q > 0.5$ ($\zeta < 1$): under damped system, roots are complex conjugate

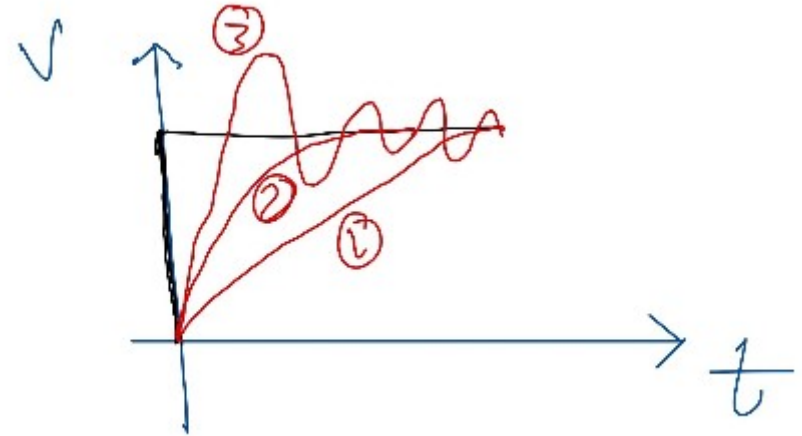Problems:

- Increase settling time
- Overshoot and undershooting which is calculated by

$$\% \text{ overshoot} = 100 e^{\frac{-\pi}{\sqrt{4Q^2 - 1}}}$$



Ringing and Peaking

- Ringing at time happens first at $Q > 0.5$ then peaking at frequency domain at $Q > 0.707$

